



University College Dublin
An Coláiste Ollscoile, Baile Átha Cliath

SEMESTER II EXAMINATIONS - 2010/2011

School of Electrical, Electronic and Mechanical Engineering

EEEN10010 Electronic & Electrical Engineering I

Professor McLaughlin

Professor Fitzpatrick

Professor Brazil

Ms. Duignan*

Time Allowed: 2 hours

Instructions for Candidates

Attempt all 15 questions in Section A and 3 out of 4 questions in Section B. Each question in Section A is worth 4 marks. Each question in Section B is worth 20 marks. The exam is worth a total of 120 marks.

Please complete Section A on a Multiple Choice Answer Sheet using a HB pencil.

Instructions for Invigilators

Please supply one Answer Book and one Multiple Choice Answer Sheet to each candidate

Non-programmable calculators are permitted.

No rough-work paper is to be provided for candidates.

Section A

Answer all of the following multiple-choice questions. Each question is worth 4 marks.

1. Electrons pass through a wire cross-section at a rate of 20×10^{12} electrons every 2 seconds. What is the current flowing in the wire?

- (A) $-0.16 \mu\text{A}$
- (B) $-1.6 \mu\text{A}$
- (C) $-32 \mu\text{A}$
- (D) $-160 \mu\text{A}$
- (E) -320 mA

2. A cylindrical conductor has a cross sectional area of 8mm^2 and is 800m long. The resistance measured between the ends of the conductor is 1.6Ω . Using the table of resistivities, Table 1, what is the metal most likely to be?

- (A) Silver
- (B) Copper
- (C) Gold
- (D) Tungsten

Material at 20°C	Resistivity (Ωm)
Silver	1.6×10^{-8}
Copper	1.72×10^{-8}
Gold	3.14×10^{-8}
Tungsten	6.28×10^{-8}

Table 1

3. Which V-I characteristic in Figure 1 below describes the behaviour of an ideal voltage source?

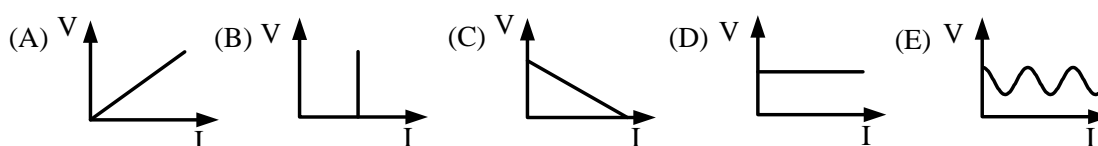


Figure 1

4. Find the average power input to a device that consumes 7200 J in 10 minutes .

- (A) 200 W
- (B) 20 W
- (C) 120 W
- (D) 1.2 W
- (E) 12 W

5. What is the voltage V in the circuit shown in Figure 2?

- (A) 1.5 V
- (B) 2 V
- (C) 2.5 V
- (D) 3 V
- (E) 4.5 V

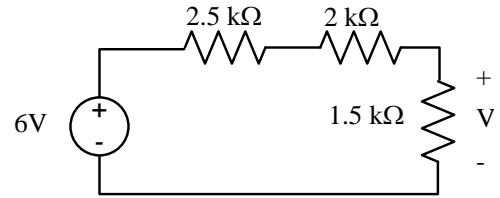


Figure 2

6. What is the current flowing in the 2.5 kΩ resistor in the circuit shown in Figure 3?

- (A) 12 μ A
- (B) 16 μ A
- (C) 12 mA
- (D) 16 mA
- (E) 20 mA

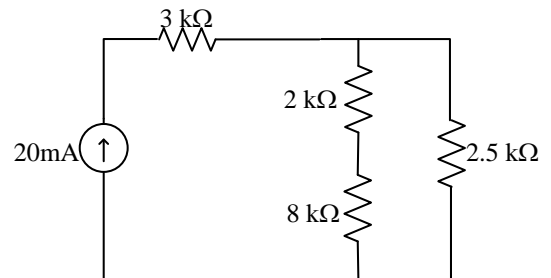


Figure 3

7. In the circuit in Figure 4 what is the power dissipated in the 20kΩ resistor?

- (A) 0.6 W
- (B) 6 W
- (C) 18 W
- (D) 1.8 W
- (E) 0.18 W

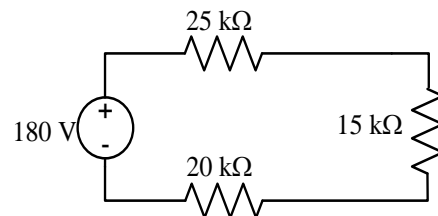


Figure 4

8. What is decimal number 110 in binary format?

- (A) 1110101
- (B) 1010111
- (C) 1011101
- (D) 1100101
- (E) 1101110

9. What is the sum of binary numbers 100100 and 110101?

- (A) 1110110
- (B) 1010101
- (C) 1011001
- (D) 1000101
- (E) 1101010

10. Which of the logic circuits shown in Figure 5 can be used to implement the exclusive-OR (XOR) operation?

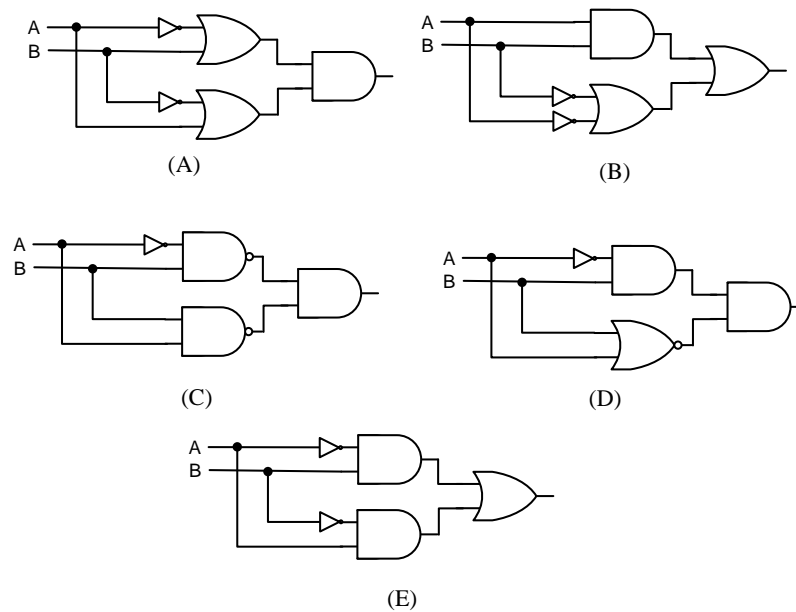


Figure 5

11. An electron is moving to the right between the poles of a magnet, as shown in Figure 6. In which direction will the electron be deflected by the magnetic field?

- (A) Into the page
- (B) Out of the page
- (C) To the left
- (D) Upwards
- (E) Downwards

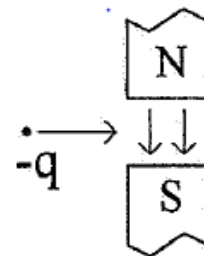


Figure 6

12. Which signal best describes the frequency spectrum shown in Figure 7?

- (A) $v(t) = 2\sin(200\pi t) + 3\sin(400\pi t) + 5\sin(100\pi t)$
- (B) $v(t) = 5\sin(200\pi t) + 3\sin(400\pi t) + 5\sin(800\pi t)$
- (C) $v(t) = 5\sin(100\pi t) + 3\sin(200\pi t) + 2\sin(400\pi t)$
- (D) $v(t) = 3\sin(200\pi t) + 5\sin(400\pi t) + 2\sin(1000\pi t)$
- (E) $v(t) = 5\sin(200\pi t) + 3\sin(400\pi t) + 2\sin(800\pi t)$

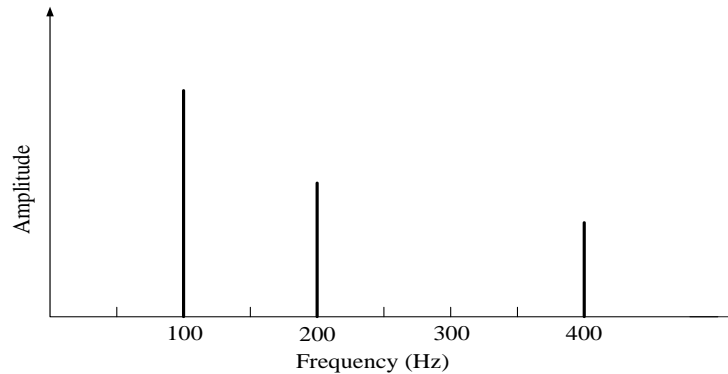


Figure 7

13. In order to select the component with the largest amplitude and eliminate the other components, the signal in Figure 7 should be passes through which of the following?

- (A) A Low Pass Filter (B) A Band Pass Filter (C) A Band Stop Filter
- (D) A High Pass Filter (E) An Amplifier

14. Figure 8 illustrates the Right Hand Grip Rule, where the right hand is gripped around a conductor as shown. Which of the following statements is true?

- (A) The thumb points in the direction the current and the fingers show the direction of the magnetic field.
- (B) The thumb shows the direction the magnetic field and the fingers point in the direction of the current.
- (C) Both the thumb and the fingers show the direction of the magnetic field.
- (D) The thumb points in the direction of the magnetic field and the fingers point in the direction of the force.



Figure 8

15. What is Boolean Algebra?

- (A) The force experienced by a charge in a magnetic field.
- (B) How any logic function can be implemented using only OR and NOT gates, or AND and NOT gates.
- (C) The observation that the density of transistors on integrated circuits doubles every two years.
- (D) The mathematics associated with the binary number system and the general field of logic.
- (E) The relationship between current and voltage for an ideal resistor.

Section B

Answer *three* of the following four questions. Each question is worth 20 marks.

16. (a) Find the Thévenin equivalent resistance of the circuit shown in Figure 9.
- (b) Find the Thévenin equivalent voltage of the circuit shown in Figure 9.
- (c) Draw the Thévenin equivalent circuit of the circuit shown in Figure 9.
- (c) An unknown load R is connected between terminals A and B in Figure 9. Calculate the value of this load R given that the load draws 0.5mA of current.

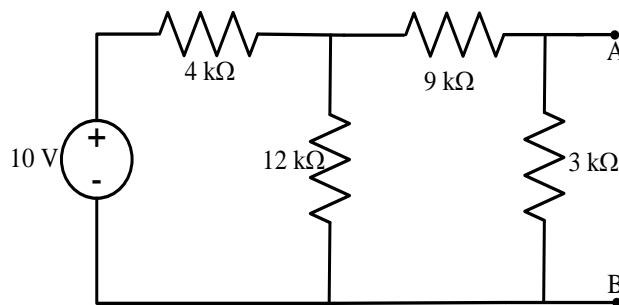


Figure 9

17. (a) Draw the Karnaugh Map for the logic function X defined in Table 2.
- (b) Find the minimum expression for the logic function X.
- (c) Draw a logic circuit to realise this function using AND, OR and NOT gates.
- (d) Using De Morgan's Laws, show how this function could also be implemented using just NOT and NAND gates. Draw a diagram of your circuit.

A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Table 2

18. (a) A wire of length ℓ carrying current I sits in a uniform magnetic field with magnetic flux density B , as shown in Figure 10. Using Lorenz's force law, $F = QuB\sin(\theta)$, show that the force felt by the wire is $F = I\ell B$.

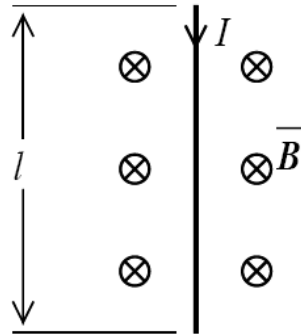


Figure 10

(b) Figure 11(a) shows a rectangular coil, which consists of 5 turns. The coil is placed in a region of uniform magnetic flux density, B , perpendicular to the plane of the coil as shown. The flux density changes as a function of time according to Figure 11(b).

- Draw a graph of the total flux, $\phi(t)$, through the coil as a function of time from 0 ms to 6 ms.
- Draw a graph of the voltage, $v(t)$, between the ends of the coil over the same time interval.

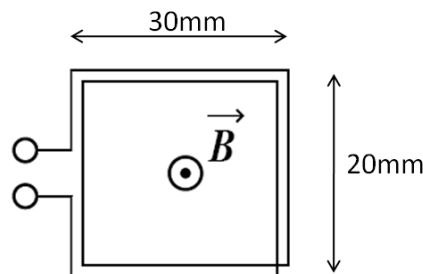


Figure 11(a)

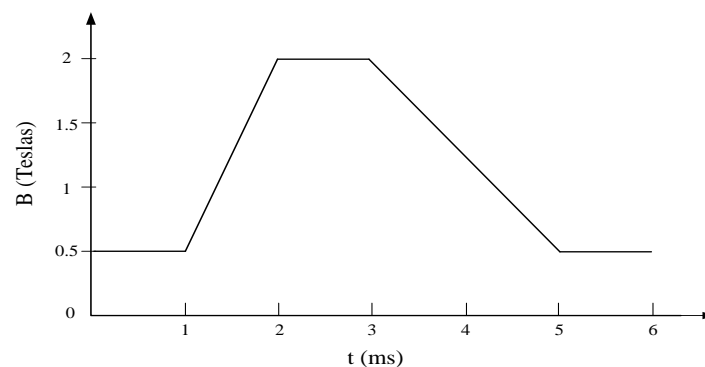


Figure 11(b)

19. (a) The inputs and outputs of a Half Adder are shown in Figure 12. Write Boolean expressions for S and C in terms of A and B that describe the Half Adder.

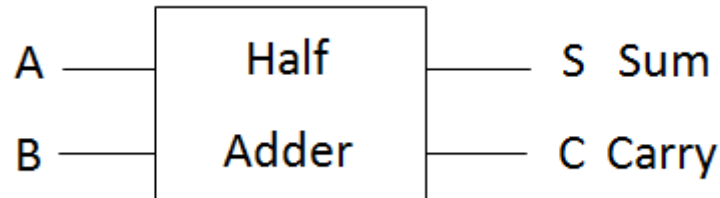


Figure 12

- (b) A signal is described by $v(t) = 5 + 3 \sin(50\pi t)$
- If $v(t)$ is sampled every 4 ms starting at $t=0$, what are the first 4 sample values?
 - If $v(t)$ is sampled every 20 ms starting at $t=0$, what are the first 4 sample values? Comment on your answer.

Formulae

The symbols below have their usual meanings.

$\vec{F} = Q\vec{E}$	$R = \frac{L}{\sigma A}$	$\overline{\overline{A}} = A$	$A + B = B + A$	$A + A \cdot B = A$
$W = QV$	$V = RI$	$A \cdot A = A$	$A \cdot B = B \cdot A$	$A \cdot (A + B) = A$
$I = \frac{dq}{dt}$	$\frac{V_2}{V_1} = \frac{N_2}{N_1}$	$A \cdot \overline{A} = 0$	$A + (B + C) = (A + B) + C$	$A + \overline{A} \cdot B = A + B$
$P = VI$	$\vec{F} = Q(\vec{u} \times \vec{B})$	$A \cdot 0 = 0$	$A \cdot (B \cdot C) = (A \cdot B) \cdot C$	$A \cdot (\overline{A} + B) = A \cdot B$
$\vec{J} = \sigma \vec{E}$	$F = BLI$	$A \cdot 1 = A$	$A \cdot (B + C) = A \cdot B + A \cdot C$	$\overline{\overline{A} \cdot B} = \overline{A} + \overline{B}$
$ \vec{E} = \frac{V}{L}$	$v = N \frac{d\phi}{dt}$	$A + A = A$	$A + (B \cdot C) = (A + B) \cdot (A + C)$	$\overline{\overline{A} + B} = \overline{A} \cdot \overline{B}$
$ \vec{J} = \frac{I}{A}$	$ \vec{B} = \frac{\phi}{A}$	$A + \overline{A} = 1$	$A + 0 = A$	$A + 1 = 1$
$G = \frac{\sigma A}{L}$	$ \vec{B} = \frac{\mu I}{2\pi d}$	$I = GV$	$ \vec{B} = \frac{\mu NI}{l}$	Charge on electron = $-1.6 \times 10^{-19} \text{C}$

“oOo”